



Cambridge International Examinations
Cambridge Pre-U Certificate

PHYSICS (PRINCIPAL)

9792/02

Paper 2 Written Paper

For Examination from 2016

SPECIMEN INSERT



The question in Section 2 of this paper will relate to the subject matter in this Insert. You will have received a copy of this booklet in advance of the examination.

The extracts on the following pages are taken from a variety of sources. Cambridge International Examinations does not necessarily endorse the reasoning expressed by the original authors, some of whom may use unconventional Physics terminology and non-SI units.

You should draw on all your knowledge of Physics when answering the questions.

The syllabus is approved for use in England, Wales and Northern Ireland as a Cambridge International Level 3 Pre-U Certificate.

This document consists of **7** printed pages and **1** blank page.

Extract 1: The heating effect of an alternating current

1. An alternating current (a.c.) can be represented by the equation:

$$I = I_0 \sin(2\pi ft)$$

where f is the frequency of the supply.

The heating effect depends on $I^2 R$, and so an average of I^2 is needed, not an average of I . To find the average value, you need the average value of \sin^2 as time runs on.

The graph of $\sin(2\pi ft)$ and the graph of $\cos(2\pi ft)$ look the same, except for a shift of origin. Because they are the same pattern, $\sin^2(2\pi ft)$ and $\cos^2(2\pi ft)$ have the same average as time goes on. But

$$\sin^2(2\pi ft) + \cos^2(2\pi ft) = 1$$

Therefore the average values of each of them must be $\frac{1}{2}$.

Therefore the average value of the power in an a.c. transmission system must be half of the peak power.

2. The power wasted as heat in a transmission line of resistance R is

$$I_0^2 R \sin^2(2\pi ft)$$

Fig. E1.1 is a sketch graph of $\sin^2 x$ against x .

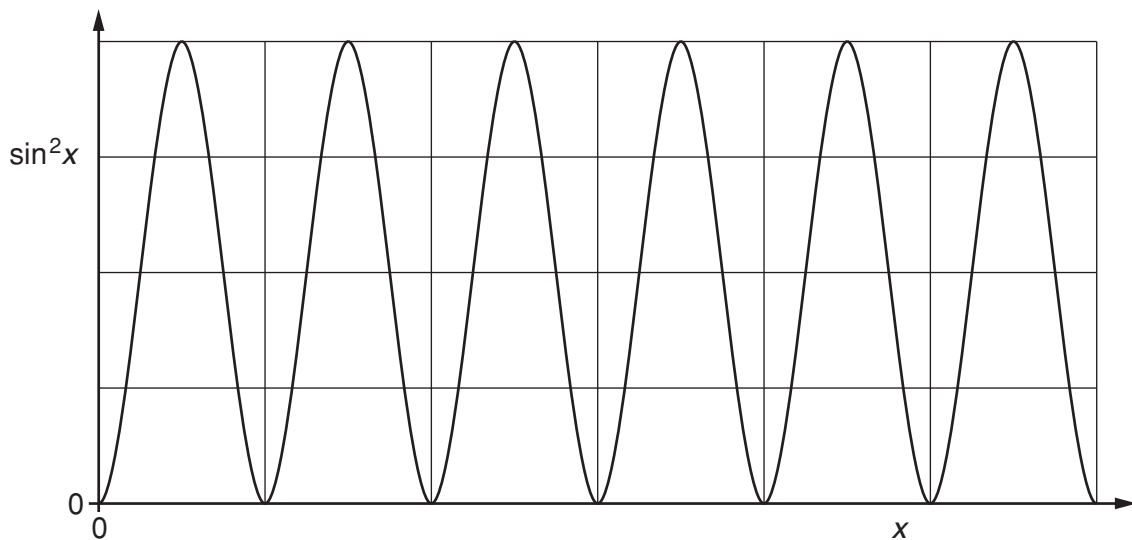


Fig. E1.1

Adapted from: http://www.practicalphysics.org/go/Guidance_107.html

Extract 2: Classic HVDC transmission



Fig. E2.1



Adapted from: <http://www.abb.com/industries/us/9AAC30300393.aspx>

Extract 3: Advantages of HVDC transmission

Awaiting copyright clearance



Adapted from: <http://www.dciinsulator.com/shownews.asp?id=155>

Extract 4: The skin effect

Awaiting copyright clearance



Adapted from: <http://www.calculatoredge.com/electronics/skin%20effect.htm>

Extract 5: Disadvantages of HVDC transmission

Awaiting copyright clearance



Adapted from: <http://www.dciinsulator.com/shownews.asp?id=155>

Extract 6: Transmission line capacitance

Long undersea high-voltage cables have a high electrical capacitance, because the conductors are surrounded by a relatively thin layer of insulation and a metal sheath. The geometry is that of a long co-axial capacitor. Where a.c. is used for cable transmission, this capacitance appears in parallel with the load. Additional current must flow in the cable to charge the cable capacitance, which generates additional losses in the conductors of the cable. Additionally, there is a dielectric loss component in the material of the cable insulation, which consumes power.

However, when d.c. is used, the cable capacitance is only charged when the cable is first energised or when the voltage is changed; there is no steady-state additional current required. For a long a.c. undersea cable, the entire current-carrying capacity of the conductor could be used to supply the charging current alone. This limits the length of a.c. cables. d.c. cables have no such limitation. Although some d.c. leakage current continues to flow through the dielectric, this is very small compared to the cable rating.

From: http://en.wikipedia.org/wiki/High-voltage_direct_current

Extract 7: Capacitive reactance

The ratio $\frac{V_0}{I_0}$, where I_0 is the peak current in the circuit and V_0 is the peak voltage, is known as the capacitive reactance. Capacitive reactance plays the same role for a capacitor that resistance does for a resistor.

The voltage V_t of an a.c. supply at time t is given by the expression

$$V_t = V_0 \sin (2\pi ft)$$

The current I_t in a circuit containing a capacitor of capacitance C is given by the expression

$$I_t = 2\pi fCV_0 \cos (2\pi ft)$$

BLANK PAGE

Copyright Acknowledgements:

Extract 1	© http://www.practicalphysics.org/go/Guidance_107.html .
Extract 2	©
Extract 3	©
Extract 4	©
Extract 5	©
Extract 6	© http://en.wikipedia.org/wiki/High-voltage_direct_current .

Awaiting copyright clearance

Permission to reproduce items where third-party owned material protected by copyright is included has been sought and cleared where possible. Every reasonable effort has been made by the publisher (UCLES) to trace copyright holders, but if any items requiring clearance have unwittingly been included, the publisher will be pleased to make amends at the earliest possible opportunity.

Cambridge International Examinations is part of the Cambridge Assessment Group. Cambridge Assessment is the brand name of University of Cambridge Local Examinations Syndicate (UCLES), which is itself a department of the University of Cambridge.